

NETWORK THEORY — GATE CHEATSHEET & SHORTCUTS

(Target: 8–10 marks with minimal effort)

1 BASIC LAWS (Free Marks Zone)

◆ KCL

Sum of currents at a node = 0

Shortcut

- Choose node with **maximum connections**
- Use **conductances** ($1/R$) → faster equations

Trap

- Forgetting current direction sign
-

◆ KVL

Sum of voltages in a loop = 0

Shortcut

- Use **mesh analysis** when loops < nodes
 - Assign mesh current clockwise always
-

2 NODAL vs MESH — WHICH TO USE?

Condition	Use
More current sources	Nodal
More voltage sources	Mesh
Supernode present	Nodal
Supermesh present	Mesh

3 THEVENIN & NORTON (VERY HIGH YIELD)

◆ Thevenin

- V_{th} = Open-circuit voltage
- R_{th} = Resistance seen with sources killed

◆ Norton

- $I_n = \frac{V_{th}}{R_{th}}$
- $R_n = R_{th}$

Source Killing Rules

- Voltage source → **short**
- Current source → **open**

⚠ Dependent sources are NEVER killed

4 MAXIMUM POWER TRANSFER (Guaranteed Question)

◆ DC

$$R_L = R_{th}$$

◆ AC

$$Z_L = Z_{th}^*$$

(conjugate)

◆ Maximum Power

$$P_{max} = \frac{V_{th}^2}{4R_{th}}$$

Shortcut

- If asked **condition only**, don't calculate anything
-

5 SERIES & PARALLEL (Fast Recognition)

◆ Series

- Same current
- Voltages add
- $R_{eq} = R_1 + R_2$

◆ Parallel

- Same voltage
- Currents add
- $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

⚡ Current Divider

$$I_1 = I \cdot \frac{R_2}{R_1 + R_2}$$

⚡ Voltage Divider

$$V_1 = V \cdot \frac{R_1}{R_1 + R_2}$$

6 STAR-DELTA (Only If Needed)

◆ Delta → Star

$$R_A = \frac{R_{AB}R_{CA}}{R_{AB} + R_{BC} + R_{CA}}$$

Shortcut

- Only use if no direct series/parallel possible

7 FIRST-ORDER CIRCUITS (EXTREMELY IMPORTANT)

◆ Time Constant

- RC: $\tau = RC$
- RL: $\tau = \frac{L}{R}$

◆ Key Rules

- Capacitor → open circuit at steady DC
- Inductor → short circuit at steady DC

◆ Initial Conditions

- Capacitor voltage **cannot change instantly**
- Inductor current **cannot change instantly**

◆ Standard Response

$$x(t) = x(\infty) + [x(0^+) - x(\infty)]e^{-t/\tau}$$

Shortcut

- At $t = \tau$: ~63% change
 - At 5τ : steady state
-

8 RLC & RESONANCE (SCORABLE)

◆ Resonant Frequency

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

◆ At Resonance

- Inductive reactance = Capacitive reactance
 - Impedance purely resistive
 - Current maximum (series RLC)
-

9 TWO-PORT NETWORKS (Recognition Based)

◆ Z-Parameters

- Open-circuit conditions
- Units: Ohms

◆ Y-Parameters

- Short-circuit conditions
- Units: Siemens

◆ ABCD Parameters

- Used for **cascade**
- Very common 1-mark questions

Shortcut

- If cascade → ABCD
 - If open terminals → Z
 - If short terminals → Y
-

10 SINUSOIDAL STEADY STATE (FAST ELIMINATION)

◆ Impedances

- Resistor: R
- Inductor: $j\omega L$
- Capacitor: $\frac{1}{j\omega C}$

◆ Power

- Real power: $P = VI \cos \phi$
- Reactive: $Q = VI \sin \phi$

EXAM HALL SHORTCUTS

- If calculation looks **long**, it's the wrong method
 - GATE loves **conditions**, not values
 - Eliminate options with **wrong units**
 - Check **DC steady state behavior** quickly
-

COMMON MISTAKES TO AVOID

- Killing dependent sources ✗
 - Forgetting capacitor/inductor behavior at DC ✗
 - Mixing RMS and peak values ✗
 - Wrong sign convention ✗
-

HOW TO USE THIS CHEATSHEET

- Morning: read once (10 min)
- Night: glance again (5 min)
- Before exam: this + formulas only