

This is a comprehensive formula sheet and collection of shortcut methods for Network Theory (Circuit Analysis), tailored for the GATE exam. It focuses on high-yield formulas and "inspection" techniques to save time.

## 1. Basics & Circuit Simplification

Concept	Formula / Condition	Shortcut / Trick
<b>KCL</b>	$\sum I_{in} = \sum I_{out}$	<b>Nodal Analysis</b> is often faster than Mesh. Total equations = $N - 1$ .
<b>KVL</b>	$\sum V_{rise} = \sum V_{drop}$	<b>Mesh Analysis</b> total equations = $B - (N - 1)$ .
<b>Star → Delta</b>	$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$ (Opposite Resistor)	If all $R$ are equal: $R_\Delta = 3R_Y$
<b>Delta → Star</b>	$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$ (Adjacent Product / Sum)	If all $R$ are equal: $R_Y = R_\Delta / 3$
<b>Source Transformation</b>	$V_s = I_s R_s$ (Series R) $\leftrightarrow$ $I_s = V_s / R_s$ (Parallel R)	Use this to reduce multiple sources into one single loop or node pair.

## 2. Network Theorems (The "Power" Tools)

### Thevenin's & Norton's Theorem

- $V_{th}$  (**Thevenin Voltage**): Open Circuit Voltage ( $V_{OC}$ ) at terminals.
- $I_N$  (**Norton Current**): Short Circuit Current ( $I_{SC}$ ) at terminals.
- $R_{th}$  (**Equivalent Resistance**): Deactivate independent sources (Voltage  $\rightarrow$  Short, Current  $\rightarrow$  Open).
- **Relationship:**  $V_{th} = I_N \times R_{th}$

**GATE Shortcut:** If the circuit has **Dependent Sources**:

1. Find  $V_{OC}$  (which is  $V_{th}$ ).

- Find  $I_{SC}$  (short the terminals).
- Calculate  $R_{th} = \frac{V_{OC}}{I_{SC}}$ . *Do not try to find  $R_{th}$  by deactivating sources if dependent sources are present unless you use the "Test Source" method ( $V_{test}/I_{test}$ ).*

## Maximum Power Transfer Theorem

Condition for  $P_{max}$  depends on the Load ( $Z_L$ ):

Source Impedance ( $Z_s$ )	Load Type ( $Z_L$ )	Condition for Max Power
Pure Resistive ( $R_s$ )	Variable $R_L$	$R_L = R_s$
Complex ( $R_s + jX_s$ )	Variable $R_L + jX_L$	$Z_L = Z_s^*$ (Conjugate)
Complex ( $R_s + jX_s$ )	Variable $R_L$ (only)	$R_L =$
<b>Max Power Value:</b>	<b>DC:</b> $P_{max} = \frac{V_{th}^2}{4R_{th}}$	<b>AC:</b> $P_{max} = \frac{1}{2} \frac{V_{th}^2}{4R_{th}}$

## 3. Transient Analysis (First Order RC / RL)

Standard Formula (The "Golden" Equation):

$$x(t) = x(\infty) + [x(0^+) - x(\infty)]e^{-t/\tau}$$

Where  $x(t)$  is either voltage  $v_C(t)$  or current  $i_L(t)$ .

Shortcut for Initial/Final Conditions:

- At  $t = 0$  (Just closed):**
  - Inductor ( $L$ ):** Acts as **Open Circuit** (Current cannot change instantly:  $i_L(0^-) = i_L(0^+)$ ).
  - Capacitor ( $C$ ):** Acts as **Short Circuit** (Voltage cannot change instantly:  $v_C(0^-) = v_C(0^+)$ ).
- At  $t = \infty$  (Steady State):**
  - Inductor ( $L$ ):** Acts as **Short Circuit** (wire).
  - Capacitor ( $C$ ):** Acts as **Open Circuit**.

### Time Constant ( $\tau$ ):

- **RC Circuit:**  $\tau = R_{eq}C$
  - **RL Circuit:**  $\tau = \frac{L}{R_{eq}}$
  - **Shortcut:** To find  $R_{eq}$ , "Look" from the capacitor/inductor terminals and **kill** all independent sources (Voltage  $\rightarrow$  Short, Current  $\rightarrow$  Open).
- 

## 4. AC Analysis & Resonance

### Resonance Formulas (Series RLC)

- **Resonant Freq:**  $\omega_0 = \frac{1}{\sqrt{LC}}$  rad/s
- **Quality Factor (Q):** Voltage Magnification.

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

- **Bandwidth (BW):**  $BW = \frac{R}{L} = \frac{\omega_0}{Q}$
- **Half Power Frequencies:**  $\omega_{1,2} = \omega_0 \pm \frac{BW}{2}$  (Approx valid if  $Q > 10$ ).
- **Impedance at Resonance:**  $Z_{min} = R$  (Purely Resistive, Unity PF).

### Resonance Formulas (Parallel RLC)

- **Resonant Freq:**  $\omega_0 = \frac{1}{\sqrt{LC}}$
- **Quality Factor (Q):** Current Magnification.

$$Q = \frac{R}{\omega_0 L} = \omega_0 RC = R \sqrt{\frac{C}{L}}$$

- **Impedance at Resonance:**  $Z_{max} = R$  (Be careful: parallel resonance has Max Impedance).
- 

## 5. Two-Port Networks (Parameters & Conditions)

Parameter	Equations	Condition for Reciprocity	Condition for Symmetry
<b>Z</b> (Impedance)	$V_1 = z_{11}I_1 + z_{12}I_2$	$z_{12} = z_{21}$	$z_{11} = z_{22}$
	$V_2 = z_{21}I_1 + z_{22}I_2$		
<b>Y</b> (Admittance)	$I_1 = y_{11}V_1 + y_{12}V_2$	$y_{12} = y_{21}$	$y_{11} = y_{22}$
	$I_2 = y_{21}V_1 + y_{22}V_2$		
<b>h</b> (Hybrid)	$V_1 = h_{11}I_1 + h_{12}V_2$	$h_{12} = -h_{21}$	$\Delta h = 1$
	$I_2 = h_{21}I_1 + h_{22}V_2$		
<b>T</b> (ABCD)	$V_1 = AV_2 - BI_2$	$AD - BC = 1$	$A = D$
	$I_1 = CV_2 - DI_2$		

### Shortcuts for Two-Port Interconnections:

- **Series Connection:** Add **Z** matrices ( $[Z] = [Z_A] + [Z_B]$ ).
- **Parallel Connection:** Add **Y** matrices ( $[Y] = [Y_A] + [Y_B]$ ).
- **Cascade Connection:** Multiply **T** matrices ( $[T] = [T_A] \times [T_B]$ ).
- **Lattice Network (Symmetric):**
  - $Z_{11} = \frac{Z_b + Z_a}{2}$ ,  $Z_{12} = \frac{Z_b - Z_a}{2}$  (where  $Z_a$  is series arm,  $Z_b$  is cross arm).

## 6. Important Tricks & Special Cases

- **Symmetry Trick:** If a network is symmetric (looks same from left and right):
  - **Horizontal Axis of Symmetry:** Potential at symmetric points is equal. You can disconnect or connect these points without changing the circuit.
  - **Vertical Axis of Symmetry:** Current distribution is symmetric.
- **Wheatstone Bridge:** If balanced ( $R_1R_4 = R_2R_3$ ), no current flows through the diagonal galvanometer/resistor. Treat it as open circuit.
- **Equivalent Inductance (Coupled):**
  - Series Aiding:  $L_{eq} = L_1 + L_2 + 2M$
  - Series Opposing:  $L_{eq} = L_1 + L_2 - 2M$
  - *Dot Convention:* Current entering dot  $\rightarrow$  Positive Mutual Inductance voltage at other dot.
- **Graph Theory:**
  - Number of Trees =  $N^{N-2}$  (for complete graph).
  - Number of Fundamental Loops =  $B - N + 1$ .
  - Number of Fundamental Cut-sets =  $N - 1$ .